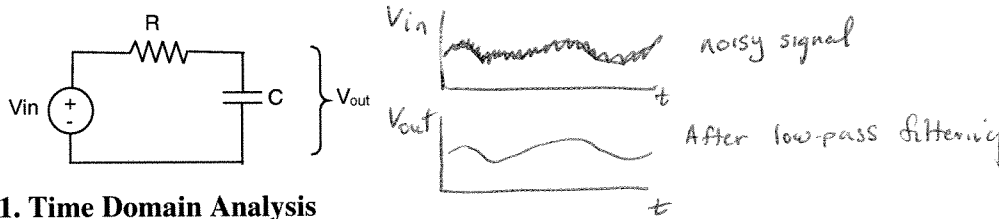


Mechanical Systems Laboratory: Lecture 3

Analysis of a 1st-order, Low-Pass Filter Circuit in the Time and Frequency Domains

The following circuit is a low-pass filter. It is useful to clean up signals with high frequency noise on it:



1. Time Domain Analysis

Let's analyze the response of this circuit to a step input

We'll use the method of undetermined coefficients to solve the differential equation. You can remember this very useful technique for linear, ordinary, differential equations using the following mnemonic:

1. Generals: set the forcing function = 0 and find the general solution to homogenous equation (don't evaluate it's coefficient yet)
2. are Particular: find the particular solution (assume particular soln is same form as forcing function)
3. about Initial Conditions: sum the homogenous and particular solutions and solve for the coefficient to the homogenous equation that satisfies the initial conditions.


$$\text{KVL: } -V_L + iR + V_C = 0$$

$$\text{Homog. } V_h = A e^{-t/\tau} \quad \tau = RC$$

$$\text{Part: } V_p = V_L \quad (\text{assume } V \text{ is a constant})$$

$$\text{Total: } V = A e^{-t/\tau} + V_L \quad \text{but } V(0) = 0 = A + V_L$$

$$V_0 = V_L (1 - e^{-t/\tau})$$

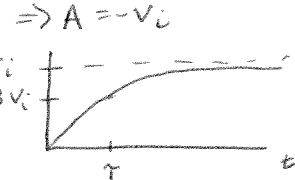

$$i = C \frac{dV_0}{dt}$$

$$RC \frac{dV_0}{dt} + V_0 = V_L$$

$$\times \frac{dV_0}{dt} = -\frac{1}{RC} V_0 + \frac{1}{RC} V_L$$

$$\text{Assume: } V_0(0) = 0, \quad V_L = \begin{cases} 0 & t < 0 \\ \text{constant} & t > 0 \end{cases}$$

$$\text{at } t = \tau \quad V_0 = V_L (1 - e^{-1}) = .63 V_L$$

Summary of important concepts:

- Method of undetermined coefficients for solving a differential equation.
- Time constant: a 1st order system has gone 63% of the way to its final value after one time constant – standard engineering technique for quantifying “how fast” a system responds.

2. Frequency Domain Analysis

Let's analyze how this system responds to a sinusoidal input. Remember: sine in \Rightarrow sine out (scaled and shifted), for a linear system. We will use three methods to find the scaling and shifting.

Method 1. Solve differential equation using method of undetermined coefficients (difficult) Assume $V_L = \sin \omega t$

Homogenous solution: $V_h = A e^{-t/\tau}$ Note: as $t \rightarrow \infty$ $V_h \rightarrow 0$ (Transient)

Particular solution: try $V_0 = a \sin(\omega t + \phi)$ where a & ϕ are unknown

$$\text{subst into } * = a \omega \cos(\omega t + \phi) = -\frac{a}{RC} \sin(\omega t + \phi) + \frac{1}{RC} \sin \omega t$$

$$\text{Useful trig. identity: } A \cos(\theta) + B \sin(\theta) = \sqrt{A^2 + B^2} \sin(\theta + \tan^{-1}(\frac{A}{B}))$$

$$a \omega \cos(\omega t + \phi) + \frac{a}{RC} \sin(\omega t + \phi) = \frac{1}{RC} \sin \omega t = \sqrt{(a \omega)^2 + (\frac{a}{RC})^2} \sin(\omega t + \phi + \tan^{-1} \omega RC)$$

for the right-most equality to hold

$$\frac{1}{RC} = \sqrt{(a \omega)^2 + (\frac{a}{RC})^2} \Rightarrow a = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

scaling

$$\phi = -\tan^{-1} \omega RC$$

phase shift

$$V_0 = a \sin(\omega t + \phi) \quad \text{with}$$

Method 2: Take Laplace Transform of differential equation that describes circuit, find the transfer function, and solve for frequency response (easier than Method 1)


Brief review of complex variables:

Complex variables keep track of two pieces of information, real and imaginary part, or magnitude and phase

Can think of complex variables as a point in the complex plane.

Can write point in Cartesian or polar coordinates. $s = \sigma + j\omega$

$$s = R e^{j\phi}$$

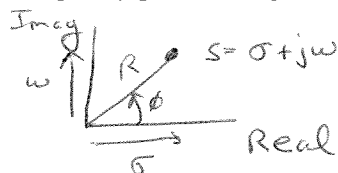

To find the magnitude in Cartesian form:

$$|s| = \sqrt{\sigma^2 + \omega^2} = R$$

To find the phase in Cartesian form:

$$\phi_s = \tan^{-1} \frac{\omega}{\sigma} = \phi$$

Magnitude of two complex variables divided by each other:

$$\left| \frac{R_1 e^{j\phi_1}}{R_2 e^{j\phi_2}} \right| = \frac{|R_1|}{|R_2|}$$

Phase of two complex variables divided by each other:

$$= \frac{R_1}{R_2} e^{j(\phi_1 - \phi_2)}$$

Now, find the transfer function and frequency response:

$$\frac{dV_o}{dt} = -\frac{1}{RC} V_o + \frac{1}{RC} V_i \quad sV_o = -\frac{1}{RC} V_o + \frac{1}{RC} V_i$$

$$\frac{V_o}{V_i} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} = \frac{1}{1 + RCs} = G(s) \quad \phi = \phi_1 - \phi_2$$

$$s = \sigma + j\omega$$

$$= R \cos \phi + j R \sin \phi$$

$$= R e^{j\phi}$$

$$\text{Euler's law } e^{j\phi} = \cos \phi + j \sin \phi$$

(can derive by Taylor's expansion)

$$|G(s)| = \frac{1}{|1 + RCj\omega|} = \frac{1}{\sqrt{1 + (RC\omega)^2}}$$

$$\phi(s) = \tan^{-1} \frac{0}{1} - \tan^{-1} \frac{RC\omega}{1}$$

$$\phi(s) = -\tan^{-1} RC\omega$$

Method 3: Use "impedances" to find transfer function (easiest)

Circuit element	Time domain	Frequency domain	Impedance
Resistor	$V(t) = RI(t)$	$V(s) = R I(s)$	R
Capacitor	$V(t) = \frac{1}{C} \int i(t) dt$	$V(s) = \frac{1}{sC} I(s)$	$\frac{1}{sC}$
Inductor	$V(t) = L di/dt$	$V(s) = sL I(s)$	sL

Note: All the usual circuit rules still hold in the frequency domain because of superposition (KVL, KCL, Op amp rules, voltage divider...). So, treat impedances like (frequency dependent) resistors in finding a circuit's transfer function.


$$V_o = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i = \frac{1}{1 + RCs} V_i \quad \frac{V_o}{V_i} = G(s) = \frac{1}{1 + RCs}$$

What do the magnitude response (i.e. scaling or attenuation factor) and phase shift response actually look like?

Fill in the following chart:

	Magnitude or Scaling	Phase
Small ω	1	0
$\omega = 1/RC = 1/\tau$	$\sqrt{\frac{1}{2}} = .707$	-45°
$\omega \Rightarrow \text{infinity}$	0	-90°

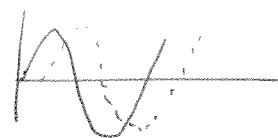So, amplitude of output is .707 x input when $\omega = \frac{1}{\tau}$



The frequency $1/\tau$ is called the "corner frequency" or "bandwidth" of the system. For this low-pass filter, input sinusoids with a frequency higher than the bandwidth are "filtered" or "attenuated".

Summary of important concepts:

- How to find a transfer function and the frequency response
- Impedances
- Corner frequency